 


# FLIP FLOPS

Binary unit capable of storing one bit – 0 or 1

Flip Flop has two stable states and a transition between these two states .

Transition is depended on input.




Transition between states

Jyoti Lakhani

# Types of FLIP FLOPS

## FLIP FLOP

 


# RS - FLIP FLOP

## Block Diagram



# RS - FLIP FLOP


RS Latch using NOR Gate

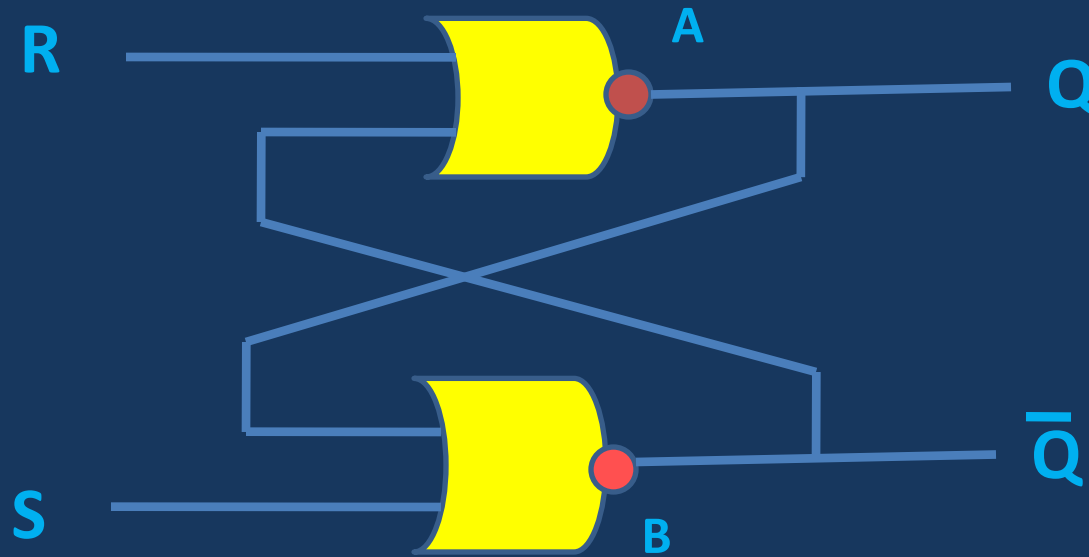

# RS - FLIP FLOP

## TRUTH TABLE

	R	S	Q
Case 1	0	0	NC
Case 2	0	1	SET
Case 3	1	0	RESET
Case 4	1	1	*

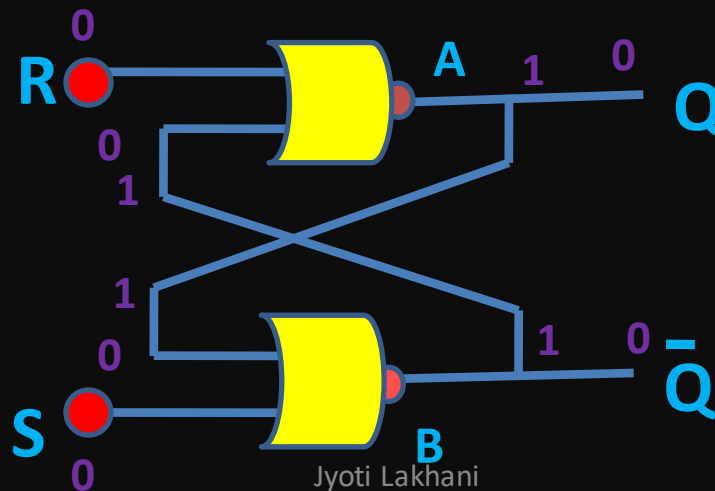


NO CHANGE

# RS - FLIP FLOP

## TRUTH TABLE


	R	S	Q
Case 1	0	0	NC
Case 2	0	1	SET
Case 3	1	0	RESET
Case 4	1	1	*

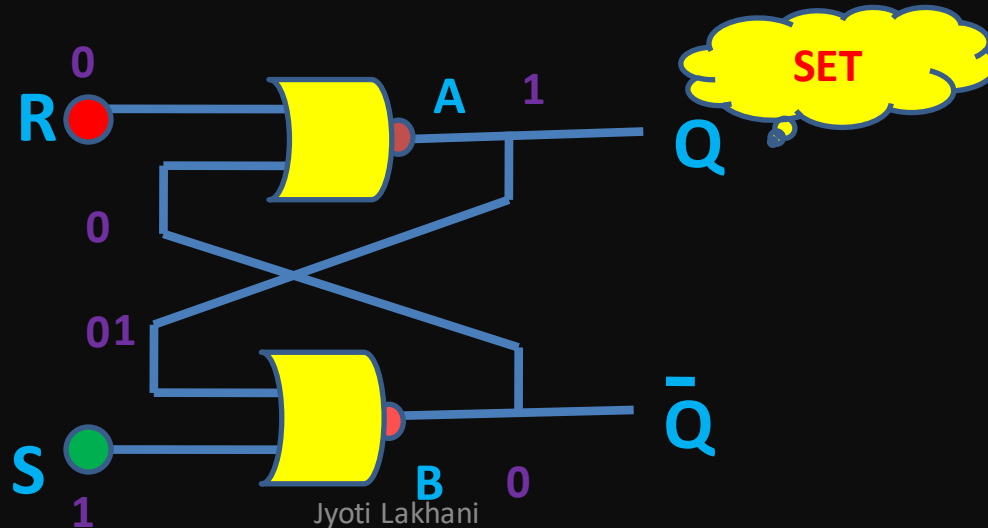

# RS - FLIP FLOP

## TRUTH TABLE


	R	S	Q
Case 1	0	0	NC
Case 2	0	1	SET
Case 3	1	0	RESET
Case 4	1	1	*

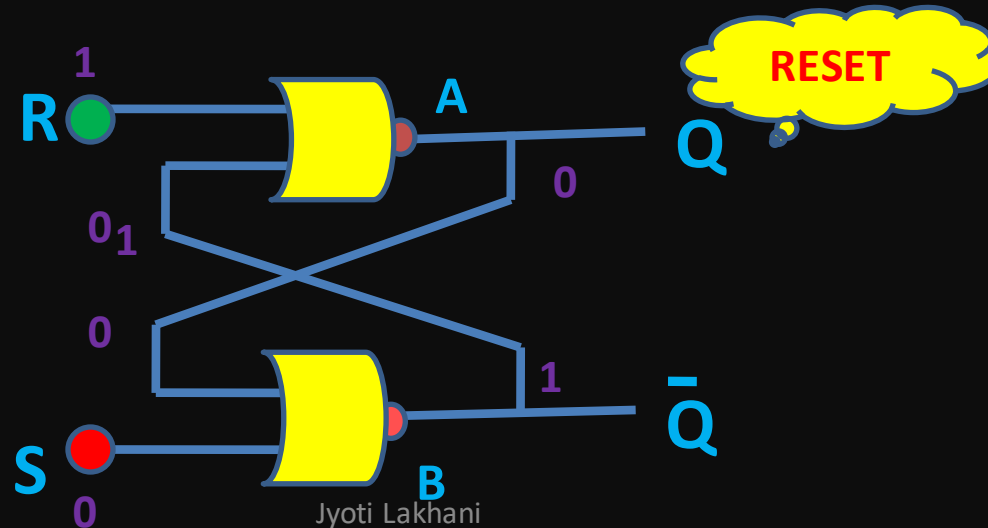

# RS - FLIP FLOP

## TRUTH TABLE

	R	S	Q
Case 1	0	0	NC
Case 2	0	1	SET
Case 3	1	0	RESET
Case 4	1	1	*

 


RACE  
CONDITION


 
# $\bar{R}\bar{S}$ - FLIP FLOP


RS Latch using NAND Gate ( $\bar{R}\bar{S}$  Flip Flop)



$\bar{R}$	$\bar{S}$	Q
0	0	*
0	1	SET
1	0	RESET
1	1	NC

# $\bar{R}\bar{S}$ - FLIP FLOP


## RS Latch using NAND Gate

 

$\bar{R}$	$\bar{S}$	Q
0	0	*
0	1	SET
1	0	RESET
1	1	NC
 
# $\bar{R}\bar{S}$ - FLIP FLOP


RS Latch using NAND Gate ( $\bar{R}\bar{S}$  Flip Flop)



$\bar{R}$	$\bar{S}$	Q
0	0	*
0	1	SET
1	0	RESET
1	1	NC

# $\bar{R}\bar{S}$ - FLIP FLOP


## RS Latch using NAND Gate

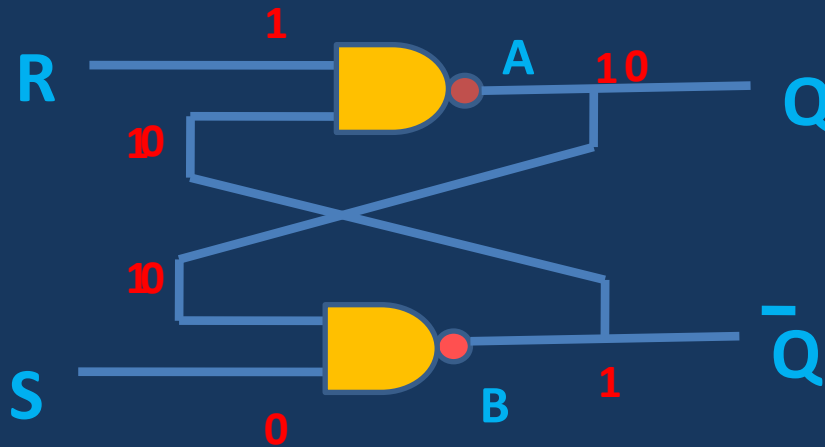

$\bar{R}$	$\bar{S}$	Q
0	0	*
0	1	SET
1	0	RESET
1	1	NC

# $\bar{R}\bar{S}$ - FLIP FLOP

## RS Latch using NAND Gate

 

$\bar{R}$	$\bar{S}$	Q
0	0	*
0	1	SET
1	0	RESET
1	1	NC

# Clocked RS Flip Flop

What is the Difference ????


A Clock signal is added to the input

What Clock Signal will do ????

Clock Signal controls the instant at which flip flop changes the state


How to Design ???

 Basic NOR- Flip Flop + Two AND Gates + A Clock Signal



# Clocked RS Flip Flop

Block Diagram of Clocked RS Flip Flop

 

**Rule of RS Flip Flop :**  $\bar{Q}$  is always complement of Q

# TRUTH TABLE


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION	Case
0	0	0	0	0	NC	1
			1	1	NC	2
		1	0	0	NC	3
			1	1	NC	4
0	1	0	0	0	NC	5
			1	1	NC	6
		1	0	1	SET	7
			1	1	SET	8
1	0	0	0	0	NC	9
			1	1	NC	10
		1	0	0	RESET	11
			1	0	RESET	12
1	1	0	0	0	NC	13
			1	1	NC	14
		1	0	?	ERROR	15
			1	?	ERROR	16



# Clocked RS Flip Flop

## Case 1


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
0	0	0	0	0	NC

 

# Clocked RS Flip Flop

## Case 2


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
0	0	0	1	1	NC

 

# Clocked RS Flip Flop

## Case 3


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
0	0	1	0	0	NC

 

# Clocked RS Flip Flop

## Case 4


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
0	0	1	1	1	NC

 

# Clocked RS Flip Flop

## Case 5


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
0	1	0	0	0	NC

 

# Clocked RS Flip Flop

## Case 6


R	S	CLK	$Q_n$	$Q_{n+1}$	ACTION
0	1	0	1	1	NC

 

# Clocked RS Flip Flop

## Case 7


R	S	CLK	$Q_n$	$Q_{n+1}$	ACTION
0	1	1	0	1	SET

 

# Clocked RS Flip Flop

## Case 8

R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
0	1	1	1	1	SET

 




# Clocked RS Flip Flop

## Case 9


R	S	CLK	$Q_n$	$Q_{n+1}$	ACTION
1	0	0	0	0	NC

 

# Clocked RS Flip Flop

## Case 10


R	S	CLK	$Q_n$	$Q_{n+1}$	ACTION
1	0	0	1	1	NC

 

# Clocked RS Flip Flop

## Case 11


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
1	0	1	0	0	RESET

 

# Clocked RS Flip Flop

## Case 12


R	S	CLK	$Q_n$	$Q_{n+1}$	ACTION
1	0	1	1	0	RESET

 

# Clocked RS Flip Flop

## Case 13


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
1	1	0	0	0	NC

 

# Clocked RS Flip Flop

## Case 14


R	S	CLK	$Q_n$	$Q_{n+1}$	ACTION
1	1	0	1	1	NC

 

# Clocked RS Flip Flop

## Case 15


R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
1	1	1	0	?	ERROR

 

# Clocked RS Flip Flop

## Case 16

R	S	CLK	Q <sub>n</sub>	Q <sub>n+1</sub>	ACTION
1	1	1	1	?	ERROR

 

Jyoti Lakhani



# D – Flip Flop (Delay Flip Flop) (Clocked)

1. Stores digital info
2. Has Single input
3. It does not have Race Condition

D Flip Flop = One RS Latch + One Inverter




# D – Flip Flop (Delay Flip Flop) (Clocked)

## D Flip Flop using NAND Gate

When Clock is **LOW** : AND gates of Flip Flop are **ENABLE**

When Clock is **HIGH** : AND gates of Flip Flop are **DISABLE**


Single Input

 

# D – Flip Flop (Delay Flip Flop) (Clocked)

## Truth Table


Clock	Input ( D )	Output (Q)
1	0	0
1	1	1
0	x	No Change

 

# D – Flip Flop (Delay Flip Flop) (Clocked)

## Truth Table


Clock	Input ( D )	Output (Q)
1	0	0
1	1	1
0	x	No Change

 

# D – Flip Flop (Delay Flip Flop) (Clocked)

## Truth Table


Clock	Input ( D )	Output (Q)
1	0	0
1	1	1
0	x	No Change

 

# D – Flip Flop (Delay Flip Flop) (Clocked)

## Truth Table


Clock	Input ( D )	Output (Q)
1	0	0
1	1	1
0	x	No Change

 

# D – Flip Flop (Delay Flip Flop) (Clocked)

## State Transition Diagram

Q (t)	D	Q (t+1)
0	0	0
0	1	1
1	0	0
1	1	1

 

# JK Flip Flop

- **Similar to SR Flip Flop**
- **Input J and K behaves like SET and RESET**


**When  $J = K = 1$ , the Flip Flop Output Toggles**

**If  $Q = 0$ , it switches to 1**


**if  $Q = 1$ , it switches to 0**



# JK Flip Flop using SR Flip Flop

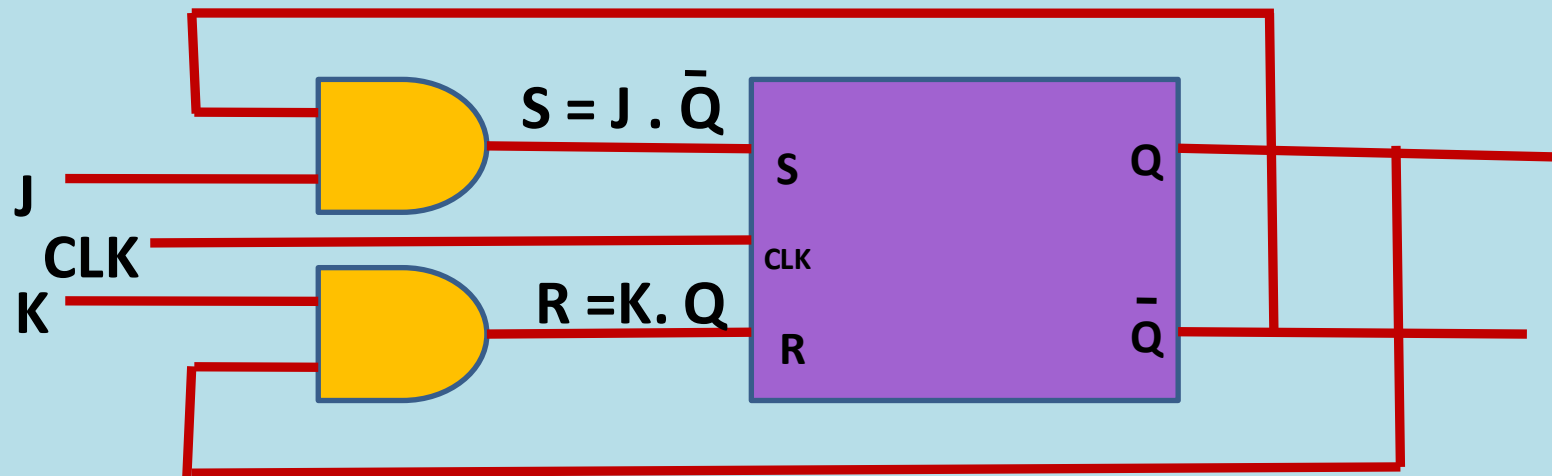


# JK Flip Flop

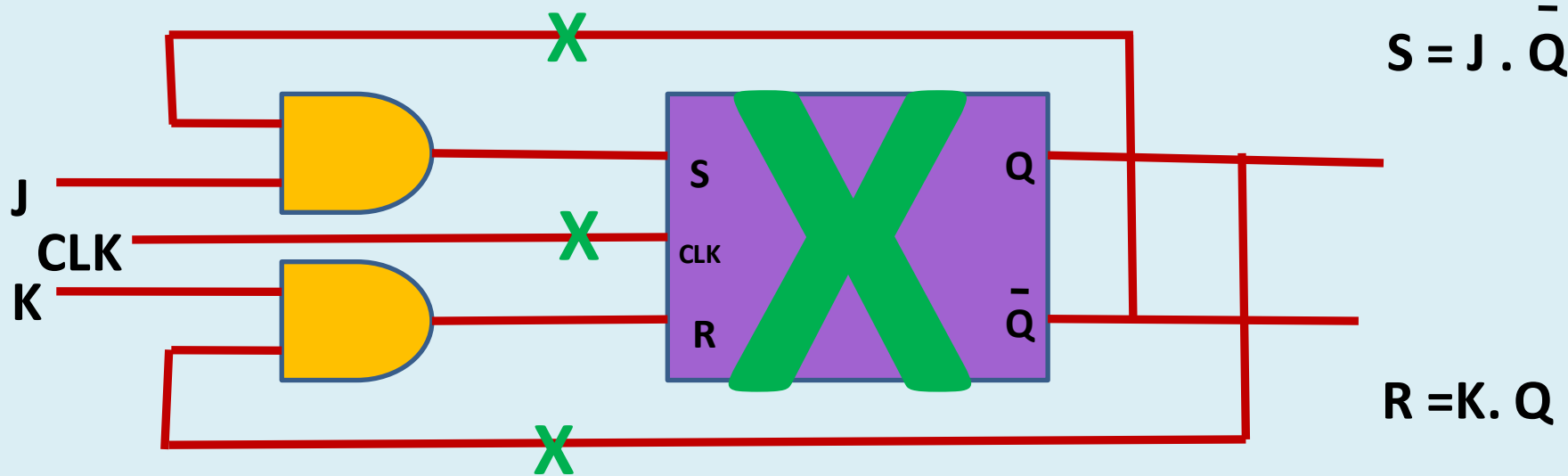


Clock	Inputs		Output $Q_{n+1}$	Action
	J	K		
X	0	0	$Q_n$	NC
1	0	1	0	RESET
1	1	0	1	SET
1	1	1	$Q_n$	TOGGLE

# JK Flip Flop

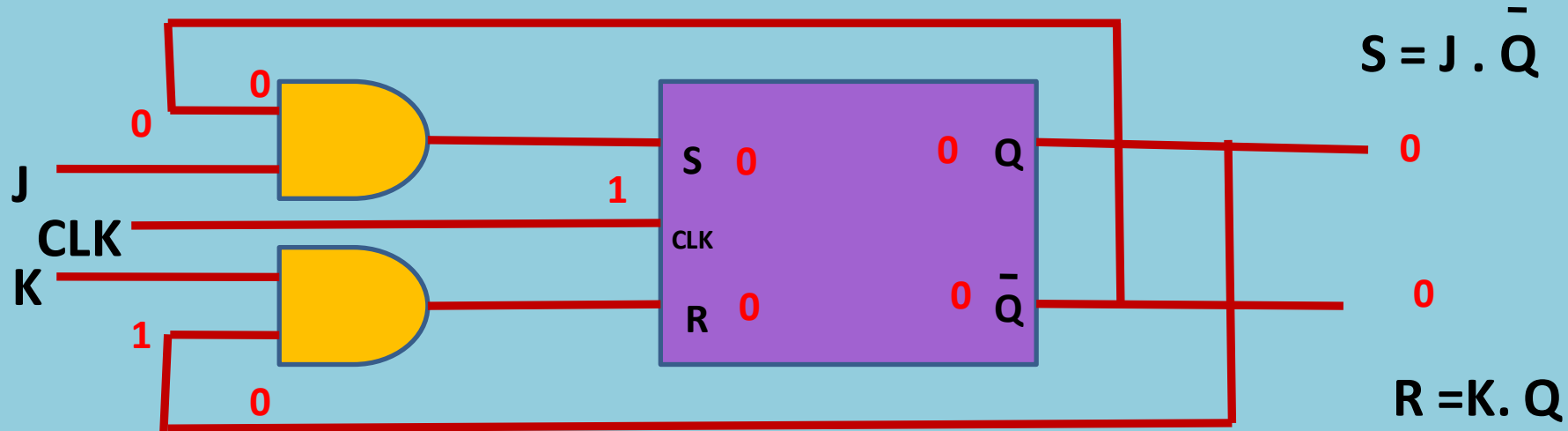


Clock	Inputs		Output Q <sub>n+1</sub>	Action
	J	K		
X	0	0	Q <sub>n</sub>	NC
1	0	1	0	RESET
1	1	0	1	SET
1	1	1	Q <sub>n</sub>	TOGGLE

# JK Flip Flop

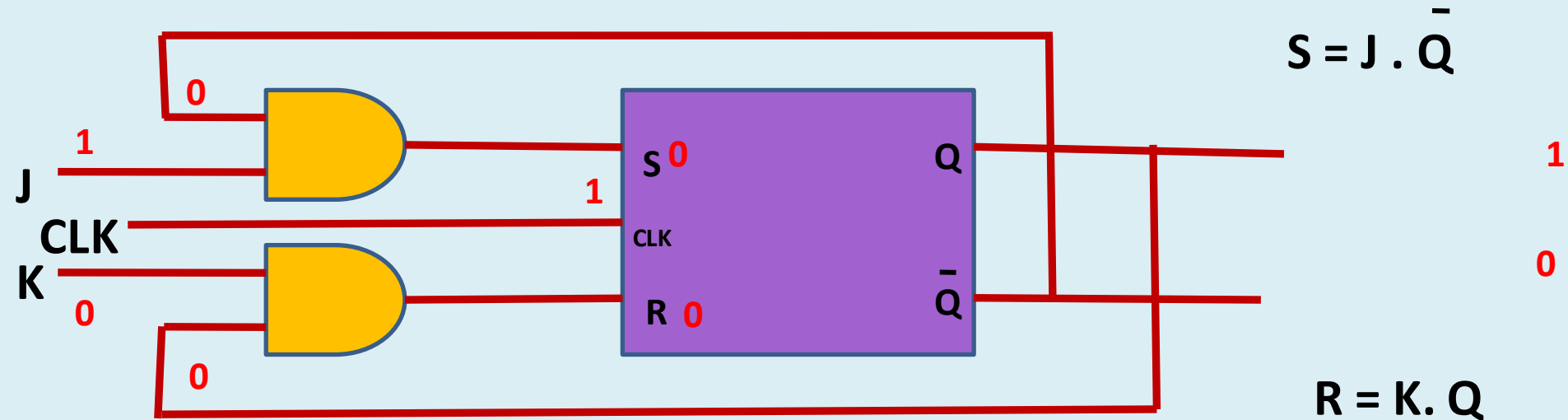

Clock	Inputs		Output $Q_{n+1}$	Action
	J	K		
X	0	0	$Q_n$	NC
1	0	1	0	RESET
1	1	0	1	SET
1	1	1	$Q_n$	TOGGLE

# JK Flip Flop

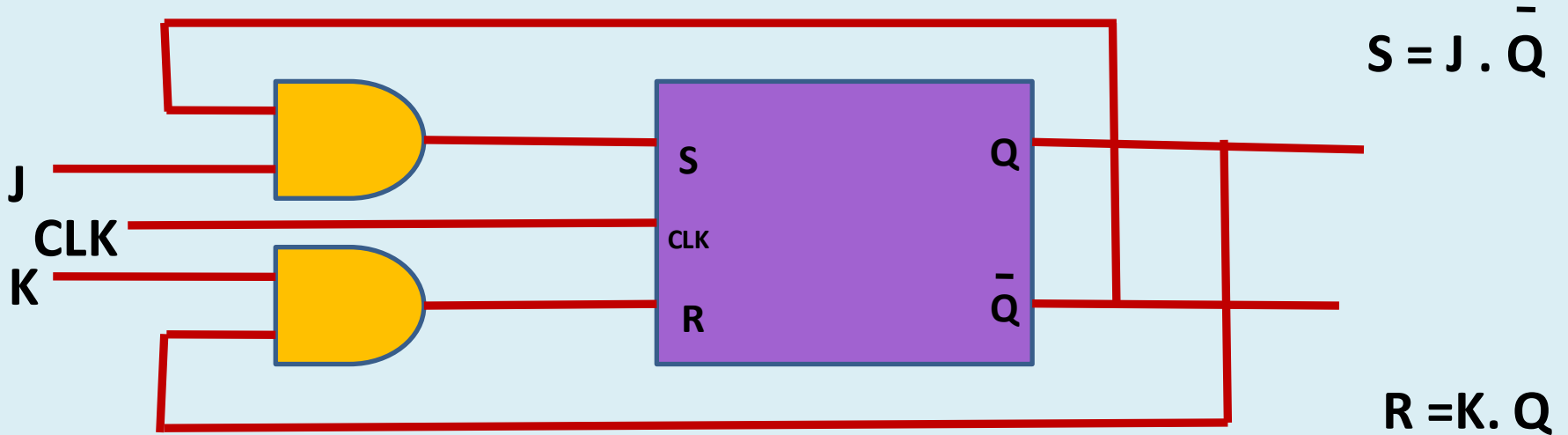

Clock	Inputs		Output $Q_{n+1}$	Action
	J	K		
X	0	0	$Q_n$	NC
1	0	1	0	RESET
1	1	0	1	SET
1	1	1	$Q_n$	TOGGLE